

BOOLEAN LOGIC

prasad deva

I. INTRODUCTION

1) *problem:* The boolean logic realized by the logic circuit is

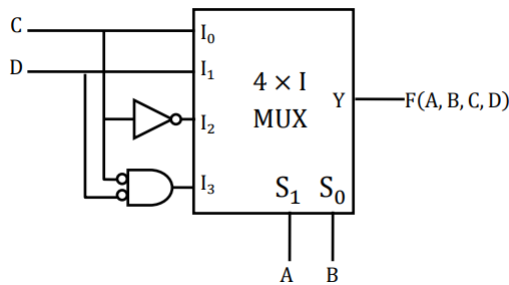


Fig. 1

II. COMPONENTS

- A. *aurdino*
- B. *bread board*
- C. *jumper wires - 10*
- D. *7 segment display*
- E. *resisitor*
- F. *7447 IC*

III. SOLUTION

The equations to be solved by using the boolean logic

$$A) F = \sum(0, 1, 3, 5, 9, 10, 14)$$

using boolean logic expression the equation expressed as

$$F = ABD + ACD + BCD + ACD$$

$$B) F = \sum(2, 3, 5, 7, 8, 12, 13)$$

using boolean expression the equation expressed as

$$F = ABC + ABD + ABC + ACD$$

using boolean expression the equation expressed as

$$C) F = \sum(1, 2, 4, 5, 11, 14, 15)$$

using boolean expression the equation expressed as

$$F = ABC + ACD + ABC + ACD$$

$$D) F = \sum(2, 3, 5, 7, 8, 9, 12)$$

using boolean expression the equation expressed as

$$F = ABC + ABD + ABC + ABCD$$

A	B	C	D	F
0	0	0	0	0
0	1	0	0	0
1	0	0	0	1
1	1	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

TABLE I: Truth Table

solution of the logic circuit is

$$F = \sum(2, 3, 5, 7, 8, 9, 12)$$

$$F = ABC + ABD + ABC + ABCD$$